模型机的 8 重 3-1 多路复用器

```
library ieee;
    use ieee.std logic 1164.all;
3 use ieee.std logic unsigned.all;
4 use ieee.std logic arith.all;
5
6 mentity zjw_8_1 is
7 mport(
8
        inl:in std logic vector (7 downto 0);
9
       enable:in std_logic_vector(3 downto 0);
10
        outl:out std_logic);
11 end zjw_8_1;
12
13 marchitecture struct of zjw 8 l is
14 Component zjw_canshuhua
16
               m:integer:=2);
   port (
17
18
               inl:in std_logic_vector(n-1 downto 0);
19
               enable:in std_logic_vector(m-1 downto 0);
20
               outl:out std logic
21
        );
22
    end component;
23
24
25
       g0:zjw canshuhua generic map(8,4) port map(inl,enable,outl);
26
    end struct;
```

参数化多路复用器

```
l library ieee;
 2
   use ieee.std logic 1164.all;
 3 use ieee.std logic unsigned.all;
 4
   use ieee.std logic arith.all;
5
 6 mentity zjw canshuhua is
8
           m:integer:=2);
9 ≣port(
10
            inl:in std_logic_vector(n-1 downto 0);
11
            enable:in std_logic_vector(m-1 downto 0);
12
            outl:out std logic
13
   );
14
   end zjw_canshuhua;
15
16 marchitecture struct of zjw canshuhua is
17
   begin
18 process(inl,enable)
19 begin
        outl<=inl(conv_integer(enable));
20
21
        end process;
   end struct;
22
```

参数化多路复用器定制为 8-1 多路复用器

```
library IEEE;
2
   use ieee.std_logic_l164.all;
3
4 mentity zjw_8_3_1 is
5 mport (
        JUMP, MOVB, MOVC: in std logic;
        in0, in1, in2: in std logic vector (7 downto 0);
8
        outl:out std_logic_vector(7 downto 0)
9 );
10 end zjw_8_3_1;
11
12 Barchitecture struct of zjw 8 3 1 is
13 begin
14
       process(in0,in1,in2,JUMP,MOVB,MOVC)
15
       begin
        if JUMP='l' then
16
               out1<=in0;
17
           elsif MOVC='1' then
18 🚍
19
               out1<=in1;
   elsif MOVB='1' then
20
21
               out1<=in2;
   22
           else
23
               out1<=in0;
           end if;
24
25 end process;
26 end struct;
```

模型机的控制信号产生逻辑

```
use ieee.std_logic_ll64.all;
     use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
    ■entity zjw kongzhixinhao is
8
          IR:in std_logic_vector(7 downto 0);
          MOVA, MOVB, MOVC, ALU, NOTO, SHR, SHL, JMP, JZ, Z, JC, C, NOP, HALT, SM:in std_logic;
10
          SME,LD_IR,DL,XL,F,FRL,FRR,CF,ZF,M,LD_PC,IN_PC,N_WE,N_CS,CFE,ZFE:out std_logic;
11
          MADD, RAA, RWBA:out std_logic_vector(1 downto 0):="00";
12
          S:out std logic vector(3 downto 0)
13
          );
      end zjw_kongzhixinhao;
14
15
   ■architecture struct of zjw_kongzhixinhao is
16
     signal command:std_logic_vector(3 downto 0);
17
18
    ■ begin
19
          command<=IR(7 downto 4);
20
          S(3)<=IR(7);
          S(2) <= IR(6);
21
          S(1)<=IR(5);
22
23
          S(0)<=IR(4);
24
         process (MOVA, MOVB, MOVC, ALU, NOTO, SHR, SHL, JMP, JZ, Z, JC, C, NOP, HALT, SM, IR)
               if SM='0' then
27
                  LD_IR<='1';
28
                   DL<='1';
                   XL<='0';
29
30
                   N_CS<='0';
                   MADD<="00";
31
32
                   LD PC<='0';
                   IN PC<='1';
33
                   N_WE<='1';
34
              elsif SM='1' then
35
                  if MOVA='1' then
36
                       RAA<=IR(1 downto 0);
37
                       RWBA<=IR(3 downto 2);
38
                       MADD<="00";
39
                       LD PC<='0';
40
                       IN PC<='0';
41
                       N WE<='0';
42
42
                        N WE<='0':
43
                        XL<='0';
44
                        DL<='1';
45
                        M<='1':
                        N_CS<='0';
46
                        F<='1':
47
                        FRR<='0':
48
                        FRL<='0';
49
                        LD_IR<='0';
50
                       CFE<='0':
51
                        ZFE<='0';
52
                        SME<='1';
53
                   elsif MOVB='1' then
    =
54
                       RAA<=IR(1 downto 0);
55
                        RWBA<="11";
56
                       MADD<="10";
57
                        LD PC<='0';
58
                        IN PC<='0';
59
                        N WE<='1';
60
                        XL<='1';
61
62
63
64
                        N_CS<='0';
                        FRR<='0';
67
                        FRL<='0';
68
                        LD IR<='0';
69
                        CFE<='0';
70
                        ZFE<='0';
                        SME<='1';
71
                   elsif MOVC='1' then
72
```

```
SME<='1';
71
                   elsif MOVC='l' then
 72
                       RAA<="11";
73
74
                       RWBA<=IR(3 downto 2);
75
76
                       MADD<="01";
                       LD PC<='0';
 77
                       IN PC<='0';
                       N WE<='0';
 79
                       XL<='0';
80
                       DL<='1';
                       M<='1';
81
82
                       N CS<='0';
83
                       F<='1';
84
                       FRR<='0';
 85
                       FRL<='0';
86
                       LD IR<='0';
87
                       CFE<='0';
88
                       ZFE<='0';
                       SME<='1';
 89
90
     elsif ALU='l' then
91
                      RAA<=IR(1 downto 0);
92
                       RWBA<=IR(3 downto 2);
93
                       MADD<="00";
                       LD_PC<='0';
94
                       IN PC<='0';
95
                       N WE<='0';
96
                       XL<='0';
97
                       DL<='0';
98
                       if command="1011" then
99
     M<='0';
100
101
     else
                          M<='1';
102
                       end if;
103
104
                       N CS<='1';
                       F<='1';
105
106
                       FRR<='0';
107
                       FRL<='0';
108
                       LD_IR<='0';
109
                       if command="1001" then
110
                           CFE<='1';
111
                           ZFE<='0';
112
     elsif command="0110" then
111
                           ZFE<='0';
                       elsif command="0110" then
112
     113
                           CFE<='0';
114
                           ZFE<='1';
115
     else
116
                           ZFE<='0';
117
                           CFE<='0';
                        end if;
118
119
                       SME<='1';
120
     elsif NOTO='1' then
121
                       RAA<=IR(1 downto 0);
122
                       RWBA<=IR(3 downto 2);
123
                       MADD<="00";
                       LD_PC<='0';
124
                       IN PC<='0';
125
                       N_WE<='0';
126
                       XL<='0';
127
                       DL<='0';
128
                       M<='1';
129
                       N_CS<='1';
130
                       F<='1';
131
                       FRR<='0';
132
                       FRL<='0';
133
                       LD IR<='0';
134
                       CFE<='0';
135
                       ZFE<='0';
136
                       SME<='1';
137
138
                   elsif SHR='1' then
    139
                       RAA<=IR(1 downto 0);
```

```
139
                        RAA<=IR(1 downto 0);
                        RWBA<=IR(3 downto 2);
140
                        MADD<="00";
141
                        LD PC<='0';
142
143
                        IN PC<='0';
144
                        N WE<='0';
145
                        XL<='0';
                        DL<='0';
146
                        M<='1';
147
148
                        N CS<='1';
149
                        F<='0';
150
                        FRR<='1':
                        FRL<='0';
151
                        LD_IR<='0';
152
                        CFE<='0';
153
                        ZFE<='0';
154
                       SME<='1';
155
                    elsif SHL='1' then
156 ■
                       RAA<=IR(1 downto 0);
157
                        RWBA<=IR(3 downto 2);
158
                        MADD<="00";
159
                        LD PC<='0';
160
                        IN PC<='0';
161
                        N WE<='0';
162
163
                        XL<='0';
                        DL<='0';
164
165
                        M<='1';
166
                        N CS<='1';
167
                        F<='0';
168
                        FRR<='0';
169
                        FRL<='1';
170
                        LD_IR<='0';
171
                        CFE<='0';
172
                        ZFE<='0';
                        SME<='1';
173
                    elsif JMP='1' or (JZ='1' and Z='1') or (JC='1'and C='1') then
174 ■
175
                       RAA<=IR(1 downto 0);
176
                        RWBA<=IR(3 downto 2);
                        MADD<="00";
177
                        LD_PC<='1';
178
                        IN PC<='0';
179
                        N WE<='1';
180
180
                        N WE<='1';
                        XL<='0';
181
182
                        DL<='1';
183
                        M<='0';
184
                        N CS<='0';
185
                        F<='0';
186
                        FRR<='0';
187
                        FRL<='0';
188
                        LD IR<='0';
189
                        CFE<='0':
                        ZFE<='0';
190
                    SME<='1';
elsif NOP='1' or (JZ='1' and Z='0') or (JC='1'and C='0') then
191
192
                        RAA<=IR(1 downto 0);
193
                        RWBA<=IR(3 downto 2);
194
                        MADD<="00";
195
                        LD PC<='1';
196
                        IN PC<='1';
197
                        N WE<='1';
198
                        XL<='0';
199
                        DL<='0';
200
201
                        M<='0';
202
                        N CS<='0';
203
                        F<='0';
204
                        FRR<='0';
205
                        FRL<='0';
206
                        LD IR<='0';
207
                        CFE<='0';
                        ZFE<='0';
208
                        SME<='1';
209
                    elsif HALT='l' then
210 🗏
```

```
elsif HALT='l' then
RAA<=IR(1 downto 0);
210 🗏
 211
212
                                     RWBA<=IR(3 downto 2);
 212
213
214
215
216
217
218
                                    MMADD<="00";

LD_PC<='0';

IN_PC<='0';

N_WE<='1';

XL<='0';

DL<='0';
                                    M<='0';
N_CS<='1';
F<='0';
FRR<='0';
 219
220
  221
  222
  223
                                     FRL<='0';
                                     LD_IR<='0';
  224
                                     CFE<='0';
ZFE<='0';
  225
  226
                                     SME<='0';
  227
  228
                              end if;
 229
230
231
                         end if;
                end process;
           end struct;
```